

Lab 6

Getting started with Vivado & VHDL


Digital System Fundamentals

Sorayut Glomglome


1. Getting Started

Basys 3 | FPGA Board




Basys 3 - Digilent Reference

 


Process Flow

 

User Interface

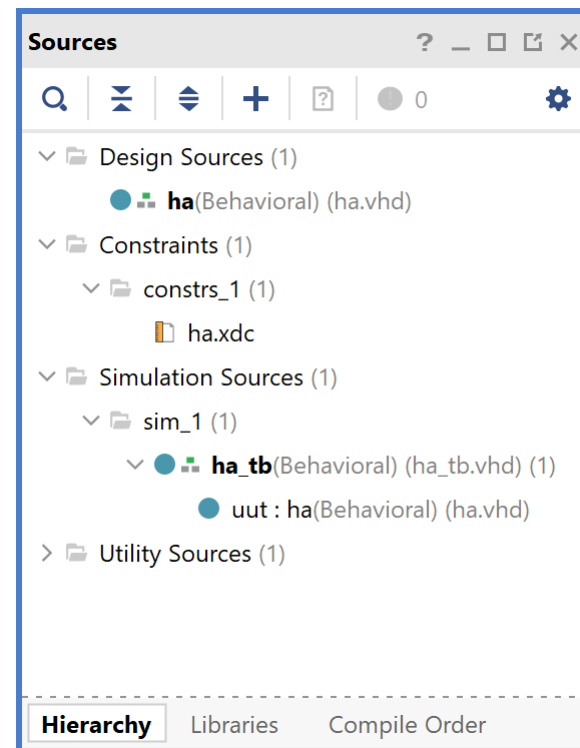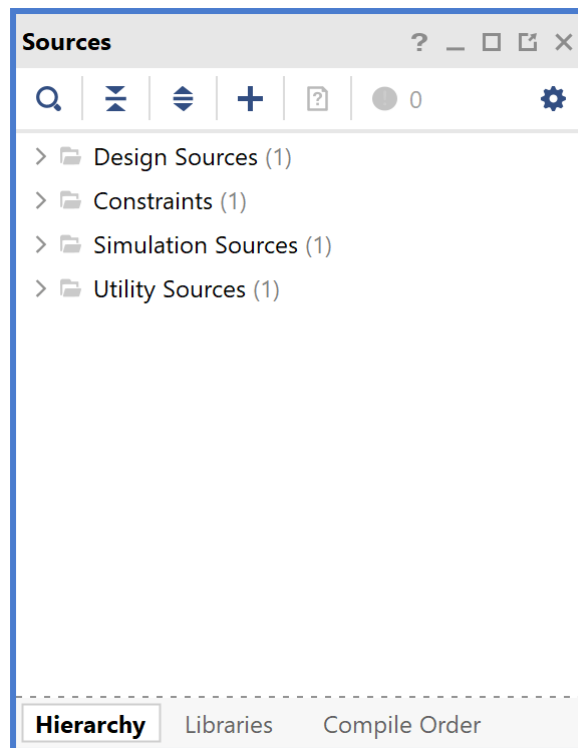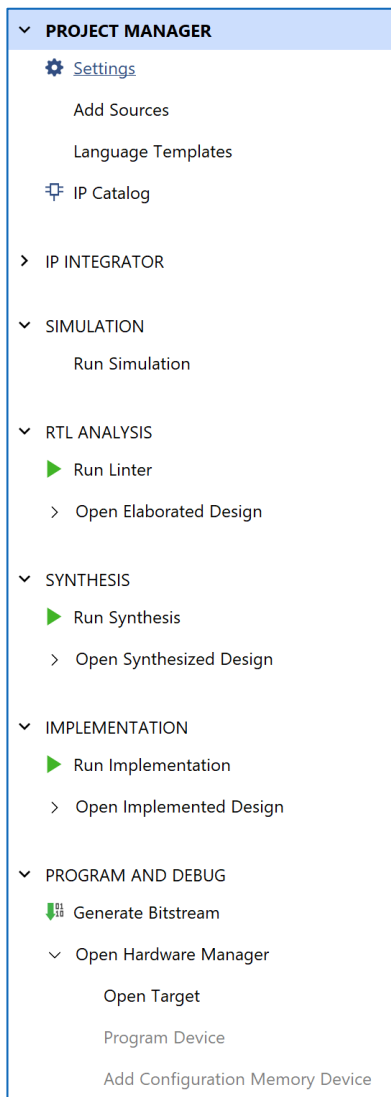


Half Adder | Block Diagram

 


Half Adder | VHDL


```
21 |
22 | library IEEE;
23 | use IEEE.STD_LOGIC_1164.ALL;
24 |
25 |
26 | entity ha is
27 |     Port ( a : in STD_LOGIC;
28 |           b : in STD_LOGIC;
29 |           sum : out STD_LOGIC;
30 |           carry : out STD_LOGIC);
31 | end ha;
32 |
33 | architecture Behavioral of ha is
34 |
35 | begin
36 |
37 |     sum <= a xor b;
38 |     carry <= a and b;
39 |
40 | end Behavioral;
41 |
```

 

Schematic

RTL ANALYSIS

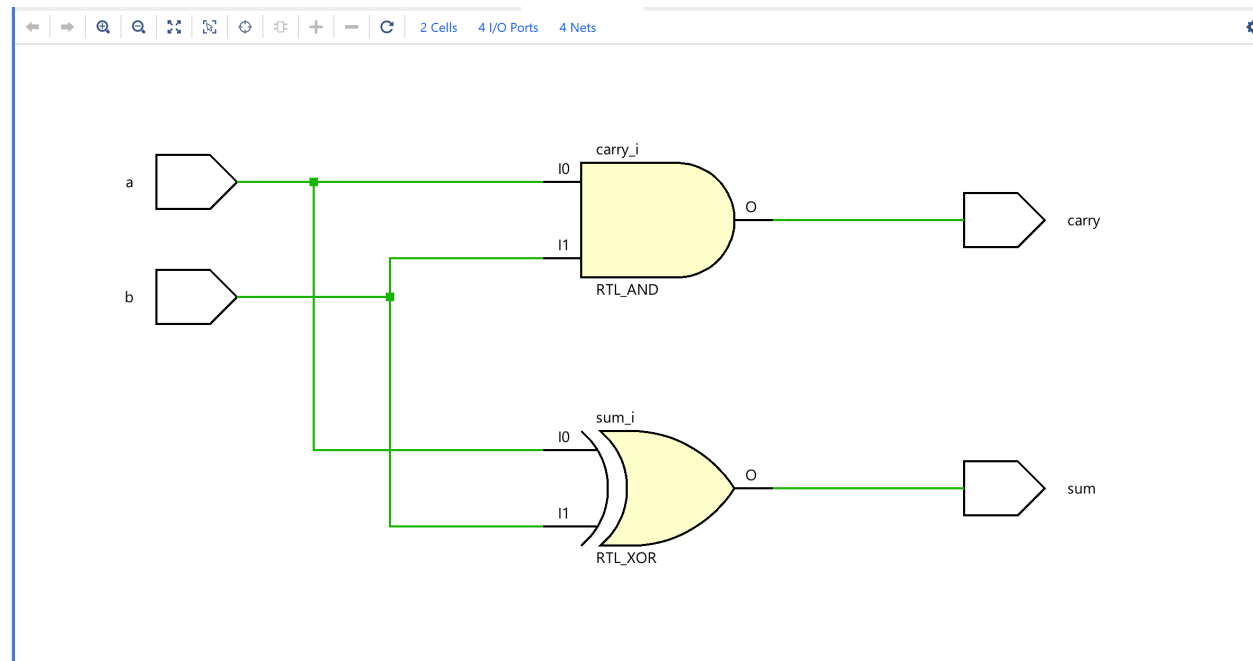- ▶ Run Linter
- ▼ Open Elaborated Design
 - ☒ Report Methodology
 - Report DRC
 - Report Noise
 -  Schematic



Tcl ConsoleMessagesLogReportsDesign RunsFind Results

Q

Name	Direction	Board Part Pin	Board Part Interface	Interface	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	
a	IN					V17			14	LVC MOS33*	3.300
b	IN					V16			14	LVC MOS33*	3.300
carry	OUT					E19			14	LVC MOS33*	3.300
sum	OUT					U16			14	LVC MOS33*	3.300

set_property PACKAGE_PIN V17 [get_ports a]

set_property PACKAGE_PIN V16 [get_ports b]

set_property PACKAGE_PIN E19 [get_ports carry]

set_property PACKAGE_PIN U16 [get_ports sum]


set_property IOSTANDARD LVCMOS33 [get_ports a]

set_property IOSTANDARD LVCMOS33 [get_ports b]

set_property IOSTANDARD LVCMOS33 [get_ports carry]


set_property IOSTANDARD LVCMOS33 [get_ports sum]

Half Adder | Testbench

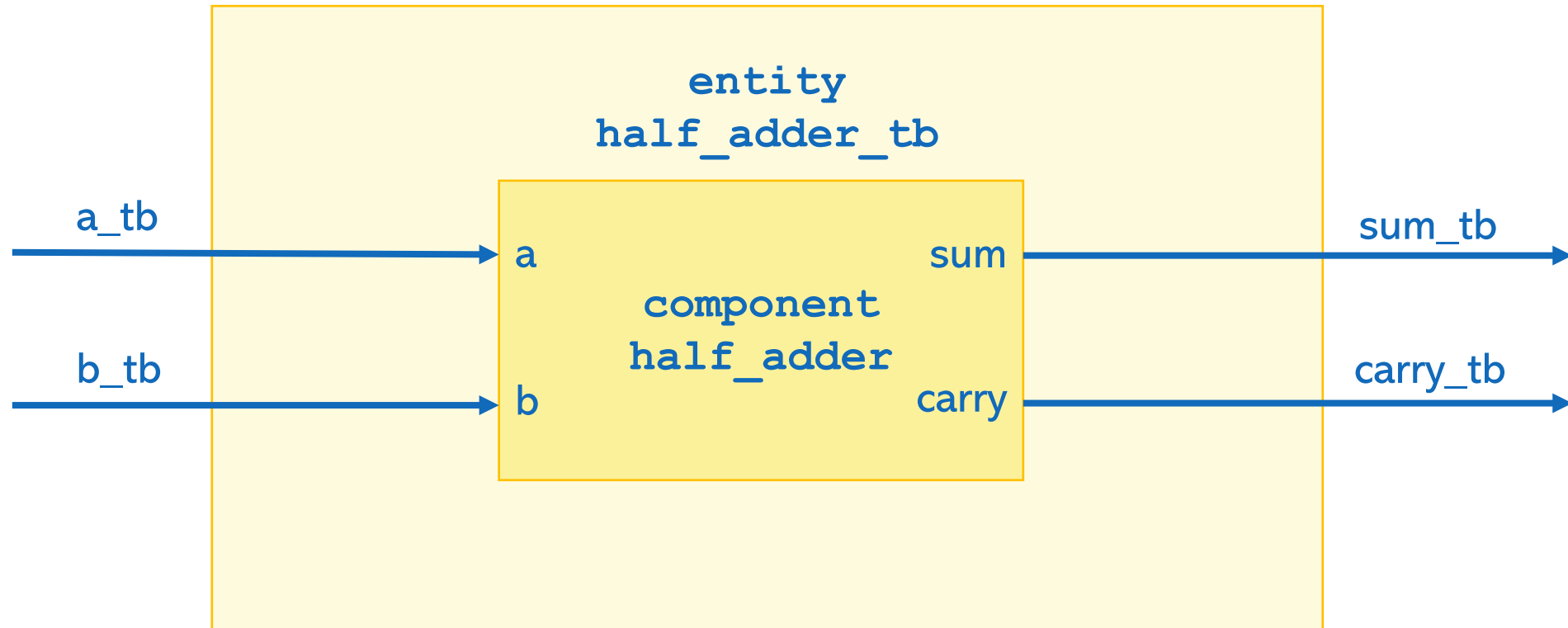

Half Adder | Testbench VHDL


```
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25
26
27
28
29
30
31
32
33
34 entity ha_tb is
35 -- Port ( );
36 end ha_tb;
37
38 architecture Behavioral of ha_tb is
39
40 component ha is port(
41     a : in STD_LOGIC;
42     b : in STD_LOGIC;
43     sum : out STD_LOGIC;
44     carry : out STD_LOGIC);
45 end component;
46
47 signal a_tb, b_tb, sum_tb, carry_tb : std_logic;
48
49 begin
50
51     uut : ha port map (a => a_tb,
52                       b => b_tb,
53                       sum => sum_tb,
54                       carry => carry_tb);
55
56     a_tb <= '0', '1' after 40 ns;
57     b_tb <= '0', '1' after 20 ns, '0' after 40 ns, '1' after 60 ns;
58
59 end Behavioral;
60
```

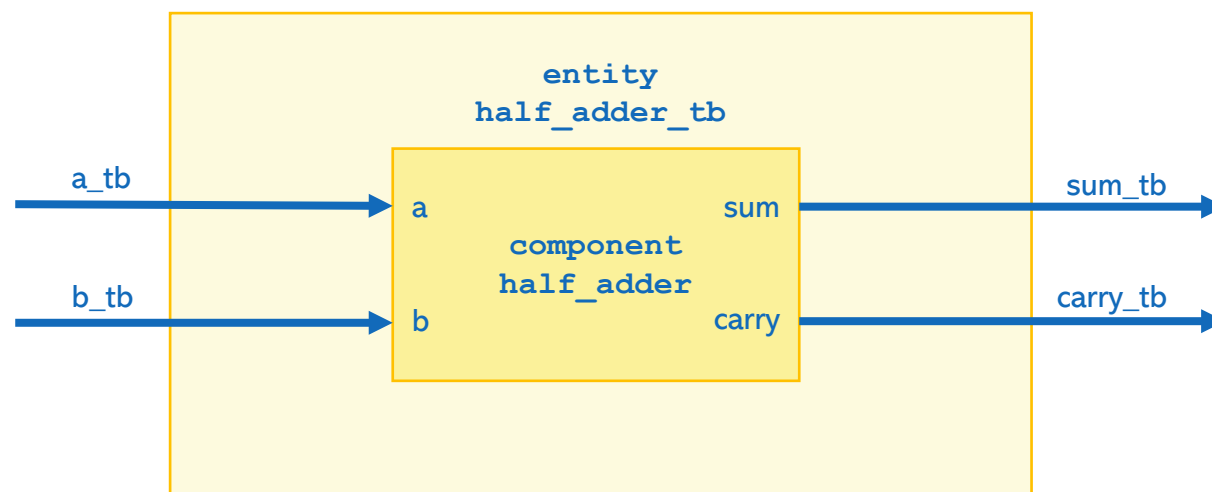


internal signal

a for 40 ns, then switch for logic 1

Half Adder | Simulation Waveform

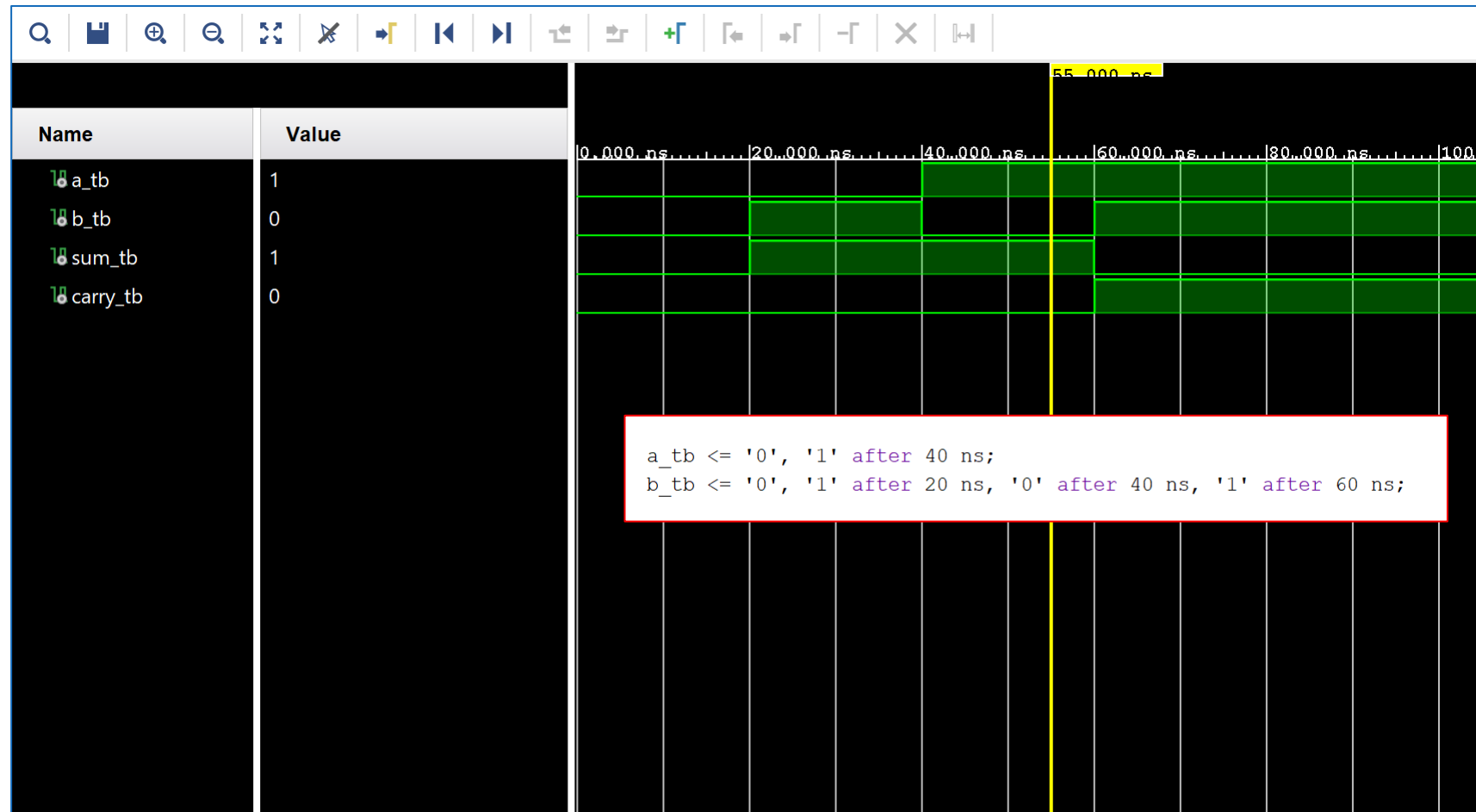

Half Adder | Add Constraints

 

```

1  ## Switches
2  set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports a]
3  set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports b]
4  #set_property -dict { PACKAGE_PIN W16 IOSTANDARD LVCMOS33 } [get_ports {sw[2]}]
5  #set_property -dict { PACKAGE_PIN W17 IOSTANDARD LVCMOS33 } [get_ports {sw[3]}]
6  #set_property -dict { PACKAGE_PIN W15 IOSTANDARD LVCMOS33 } [get_ports {sw[4]}]
7  #set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports {sw[5]}]
8  #set_property -dict { PACKAGE_PIN W14 IOSTANDARD LVCMOS33 } [get_ports {sw[6]}]
9  #set_property -dict { PACKAGE_PIN W13 IOSTANDARD LVCMOS33 } [get_ports {sw[7]}]
10 #set_property -dict { PACKAGE_PIN V2 IOSTANDARD LVCMOS33 } [get_ports {sw[8]}]
11 #set_property -dict { PACKAGE_PIN T3 IOSTANDARD LVCMOS33 } [get_ports {sw[9]}]
12 #set_property -dict { PACKAGE_PIN T2 IOSTANDARD LVCMOS33 } [get_ports {sw[10]}]
13 #set_property -dict { PACKAGE_PIN R3 IOSTANDARD LVCMOS33 } [get_ports {sw[11]}]
14 #set_property -dict { PACKAGE_PIN W2 IOSTANDARD LVCMOS33 } [get_ports {sw[12]}]
15 #set_property -dict { PACKAGE_PIN U1 IOSTANDARD LVCMOS33 } [get_ports {sw[13]}]
16 #set_property -dict { PACKAGE_PIN T1 IOSTANDARD LVCMOS33 } [get_ports {sw[14]}]
17 #set_property -dict { PACKAGE_PIN R2 IOSTANDARD LVCMOS33 } [get_ports {sw[15]}]
18
19
20 ## LEDs
21 set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports sum]
22 set_property -dict { PACKAGE_PIN E19 IOSTANDARD LVCMOS33 } [get_ports carry]
23 #set_property -dict { PACKAGE_PIN U19 IOSTANDARD LVCMOS33 } [get_ports {led[2]}]
24 #set_property -dict { PACKAGE_PIN V19 IOSTANDARD LVCMOS33 } [get_ports {led[3]}]
25 #set_property -dict { PACKAGE_PIN W18 IOSTANDARD LVCMOS33 } [get_ports {led[4]}]
26 #set_property -dict { PACKAGE_PIN U15 IOSTANDARD LVCMOS33 } [get_ports {led[5]}]
27 #set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports {led[6]}]
28 #set_property -dict { PACKAGE_PIN V14 IOSTANDARD LVCMOS33 } [get_ports {led[7]}]
29 #set_property -dict { PACKAGE_PIN V13 IOSTANDARD LVCMOS33 } [get_ports {led[8]}]
30 #set_property -dict { PACKAGE_PIN V3 IOSTANDARD LVCMOS33 } [get_ports {led[9]}]
31 #set_property -dict { PACKAGE_PIN W3 IOSTANDARD LVCMOS33 } [get_ports {led[10]}]
32 #set_property -dict { PACKAGE_PIN U3 IOSTANDARD LVCMOS33 } [get_ports {led[11]}]
33 #set_property -dict { PACKAGE_PIN P3 IOSTANDARD LVCMOS33 } [get_ports {led[12]}]
34 #set_property -dict { PACKAGE_PIN N3 IOSTANDARD LVCMOS33 } [get_ports {led[13]}]
35 #set_property -dict { PACKAGE_PIN P1 IOSTANDARD LVCMOS33 } [get_ports {led[14]}]
36 #set_property -dict { PACKAGE_PIN L1 IOSTANDARD LVCMOS33 } [get_ports {led[15]}]
37

```

Reference


1. [Step-by-step guide on how to design and implement a Half Adder using Testbench code with Xilinx Vivado design tool using VHDL. | by Radha Kulkarni | Medium](#)
2. [VHDL code for half adder & full adder using dataflow method - full code & explanation \(technobyte.org\)](#)
3. [Vivado Tutorial | Implementing Half Adder | VHDL Coding | Simulation | #FPGA #VLSI #VHDL \(youtube.com\)](#)
4. [electronics blog: VHDL half adder code test in circuit and test bench xilinx spartan 3 development board \(quartoart.blogspot.com\)](#)
5. [digilent-xdc/Basys-3-Master.xdc at master · Digilent/digilent-xdc · GitHub](#)
6. [Basys 3 - Digilent Reference](#)
7. [VHDL Tutorial: Learn by Example \(ucr.edu\)](#)

2. Experiment



Implement full adder using VHDL & Vivado

2.1 Checkpoint 1

Full Adder | Process Flow

 

Full Adder | Block Diagram & Constraints

  

Port	I/O Type	Label	Pin
a	switch	SW0	V17
b	switch	SW1	V16
cin	switch	SW2	W16
sum	LED	LD0	U16
cout	LED	LD1	E19

THANK YOU